

## 31-1 Speed Control

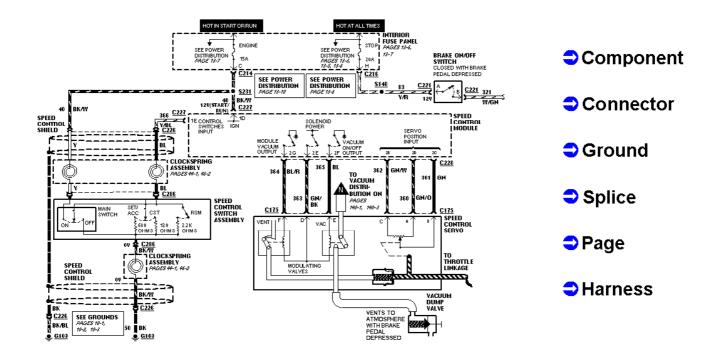

## 31-2 Speed Control

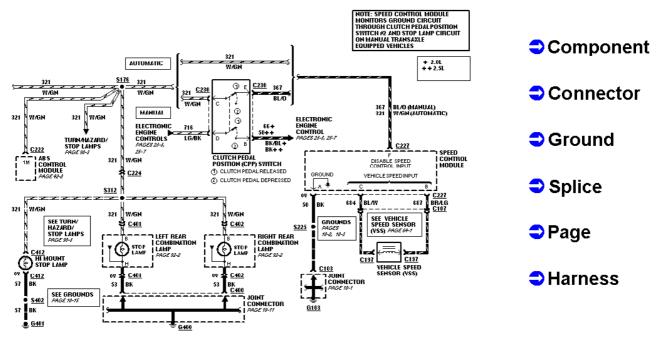

How The Circuit Works